## ALU Control

ALU control for the a 64-bit Integer ALU. The control unit takes in 2 inputs:

- (a) A 2-bit input that distinguishes the nature of operation to perform.
- (b) Minimal bits from the funct3 and funct7 bits of the instruction to identify the operation.

## TRUTH TABLE:

ALU Op		Funct - 7							Funct - 3			Ор			
0	0	X	X	X	X	X	X	X	X	X	X	0	0	1	0
X	1	X	X	X	X	X	X	X	X	X	X	0	1	1	0
1	X	0	0	0	0	0	0	0	0	0	0	0	0	1	0
1	X	0	1	0	0	0	0	0	0	0	0	0	1	1	0
1	X	0	0	0	0	0	0	0	1	1	1	0	0	0	0
1	X	0	0	0	0	0	0	0	1	1	0	0	0	0	1

The highlighted bits are the minimal bits from funct - 3 and funct - 7 to identify the operation

## **VERILOG CODE:**

```
hackspot@hackspot-inspiron-3521:~/code/Verilog/A3$ bat CU.v
         File: CU.v
                 K Rahul Reddy 17C0119
                 Sushruth V
                                17C0148
                 24 October 2018
                 funct7[5] and funct3[2:0] are required to identify operation.
         */
        module CU(output [3:0] Op, input[1:0] ALU_Op, input[6:0] funct7, input[2:0] funct3);
             wire F0 = funct3[0];
             wire F1 = funct3[1];
             wire F2 = funct3[2];
             wire F3 = funct7[5];
             assign Op[3] = 0;
             assign Op[2] = ALU_Op[0] | (ALU_Op[1] & F3 & ~F2 & ~F1 & ~F0);
             assign Op[1] = \sim F1 \mid \sim ALU_Op[1];
             assign Op[0] = ALU_Op[1] \& F1 \& ~F0;
         endmodule
```

## **OUTPUT:**

```
hackspot@hackspot-inspiron-3521:~/code/Verilog/A3$ iverilog -o tb_CU.vvp tb_CU.v
hackspot@hackspot-inspiron-3521:~/code/Verilog/A3$ vvp tb_CU.vvp
VCD info: dumpfile CU.vcd opened for output.
Case 0: Add(ALU_Op code)
ALU_Op = 00 funct7 = 0100111 funct3 = 111
Opcode = 0010
Case 1: Subtract(ALU_Op code)
ALU_Op = 01
                                  funct7 = 0000000
                                                                                funct3 = 111
Opcode = 0110
Case 2: Add(R-type)
ALU_Op = 10
                                  funct7 = 0000000
                                                                                funct3 = 000
Opcode = 0010
Case 3: Subtract(R-type)

10 funct7 = 0100000
                                                                                funct3 = 000
Opcode = 0110
Case 4: And(R-type)
ALU_Op = 10
                                  funct7 = 0000000
                                                                                funct3 = 111
Opcode = 0000
Case 5: Or(R-type)
ALU_Op = 10
                                  funct7 = 0000000
                                                                                funct3 = 110
Opcode = 0001
```