


3. Half Adder

The circuit is used to add two 1-bit values to give corresponding 1-bit sum and carry outputs.

Truth table:

Truth Table			
Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Block Diagram:

 

Verilog Code:

```
File: halfAdder.v
1  /*
2      K Rahul Reddy    17C0119
3      Sushruth V      17C0148
4      15 October 2018
5  */
6
7
8  module halfAdder (output reg sum, output reg carry, input op1, input op2);
9      always @ (op1 or op2) begin          //if inputs are 0 and 0, thread is not executed
10         sum = op1 ^ op2;                  // sum bit of two operands
11         carry = op1 & op2;                 // carry bit of two operands
12     end
13 endmodule
```

Explanation:

The above block diagram is coded in the module using data flow modelling.

Output:

```
VCD info: dumpfile tb_halfAdder.vcd opened for output.
Sum of 1 and 1
Sum = 0
Carry = 1

Sum of 1 and 0
Sum = 1
Carry = 0

Sum of 0 and 1
Sum = 1
Carry = 0

Sum of 0 and 0
Sum = 0
Carry = 0
```